

Contents

- 1 Overview6**
- 2 GE863 module connections7**
 - 2.1 PIN-OUT7
 - 2.2 PINS LAYOUT 10
- 3 Hardware Commands 11**
 - 3.1 Turning ON the GE863-QUAD/PY 11
 - 3.2 Turning OFF the GE863-QUAD/PY 12
 - 3.2.1 Hardware shutdown 13
 - 3.3 Hardware Unconditional Reboot..... 13
- 4 Power Supply 15**
 - 4.1 Power Supply Requirements 15
 - 4.2 General Design Rules 16
 - 4.2.1 Electrical design Guidelines..... 16
 - 4.2.1.1 + 5V input Source Power Supply Design Guidelines 16
 - 4.2.1.2 + 12V input Source Power Supply Design Guidelines 17
 - 4.2.1.3 Battery Source Power Supply Design Guidelines 18
 - 4.2.1.4 Battery Charge control Circuitry Design Guidelines 19
 - 4.2.2 Thermal Design Guidelines 20
 - 4.2.3 Power Supply PCB layout Guidelines 21
- 5 Antenna.....22**
 - 5.1 GSM Antenna Requirements.....22
 - 5.2 GSM Antenna - PCB line Guidelines23
 - 5.3 GSM Antenna - installation Guidelines23
- 6 Serial Ports23**
 - 6.1 MODEM SERIAL PORT24
 - 6.2 MODEM SERIAL PORT 2 (Python Debug).....26
 - 6.3 RS232 level translation.....26
 - 6.4 5V UART level translation28
- 7 Audio Section Overview30**
 - 7.1 Microphone Paths Characteristic and Requirements32
 - 7.2 General Design Rules35
 - 7.3 Other considerations35



**GE863-QUAD
GE863-PY**

1vv0300715 Rev. 1 - 19/09/06

7.4	Microphone Biasing	36
7.4.1	Balanced Microphone Biasing	36
7.4.2	Unbalanced Microphone Biasing	37
7.5	Microphone Buffering	39
7.5.1	Buffered Balanced Mic.....	39
7.5.2	Buffered Unbalanced (Single Ended) Microphone	41
8	OUTPUT LINES (Speaker).....	44
8.1	Short description.....	44
8.2	Output Lines Characteristics	45
8.3	General Design Rules	46
8.3.1	Noise Filtering.....	46
8.4	Handset Earphone Design	47
8.5	Hands-Free Earphone (Low Power) Design.....	48
8.6	Car Kit Speakerphone Design	49
8.7	The Evaluation Kit for Telit Modules EVK2.....	50
8.7.1	Short Description	50
8.7.2	EVK2 Audio Lines Characteristics.....	51
9	SIM DESIGN GUIDES	52
9.1	Data Integrity	52
9.2	EMI/EMC	52
9.3	ESD	52
9.4	SIM Supply	53
9.5	SCHEMATIC	53
9.6	LAYOUT	54
10	General Purpose I/O.....	55
10.1	Using a GPIO Pad as INPUT	55
10.2	Using a GPIO Pad as OUTPUT	55
10.3	Using the Alarm Output GPIO6.....	56
10.4	Using the Buzzer Output GPIO7.....	56
11	DAC and ADC section.....	57
11.1	DAC Converter.....	57
11.1.1	Description.....	57
11.1.2	Enabling DAC	58
11.1.3	Low Pass Filter Example	58
11.2	ADC Converter.....	59
11.2.1	Description.....	59
11.2.2	Using ADC Converter	59



GE863-QUAD
GE863-PY

1vv0300715 Rev. 1 - 19/09/06

This document is relating to the following products:

GE863-QUAD Embedded	
GE863-PY Embedded	
GE863-QUAD Pb free	3 990 250 662
GE863-PY Pb free	3 990 250 661



1 Overview

The aim of this document is the description of some hardware solutions useful for developing a product with the [Telit GE863-QUAD/PY module](#).

In this document all the basic functions of a mobile phone will be taken into account; for each one of them a proper hardware solution will be suggested and eventually the wrong solutions and common errors to be avoided will be evidenced. Obviously this document cannot embrace the whole hardware solutions and products that may be designed. The wrong solutions to be avoided shall be considered as mandatory, while the suggested hardware configurations shall not be considered mandatory, instead the information given shall be used as a guide and a starting point for properly developing your product with the [Telit GE863-QUAD/PY module](#). For further hardware details that may not be explained in this document refer to the Telit GE863-QUAD/PY Product Description document where all the hardware information is reported.

NOTICE

(EN) The integration of the GSM/GPRS GE863-QUAD cellular module within user application shall be done according to the design rules described in this manual.

(IT) L'integrazione del modulo cellulare GSM/GPRS GE863-QUAD all'interno dell'applicazione dell'utente dovrà rispettare le indicazioni progettuali descritte in questo manuale.

(DE) Die Integration des GE863-QUAD GSM/GPRS Mobilfunk-Moduls in ein Gerät muß gemäß der in diesem Dokument beschriebenen Konstruktionsregeln erfolgen

(SL) Integracija GSM/GPRS GE863-QUAD modula v uporabniški aplikaciji bo morala upoštevati projektne navodila, opisana v tem priročniku.

(SP) La utilización del modulo GSM/GPRS GE863-QUAD debe ser conforme a los usos para los cuales ha sido diseñado descritos en este manual del usuario

(FR) L'intégration du module cellulaire GE863-QUAD GSM/GPRS dans l'application de l'utilisateur sera faite selon les règles de conception décrites dans ce manuel

(HE) האינטגרציה של המודול הסלולרי GE863-QUAD עם המוצר. את ההנחיות המפורטות במסמך זה בתהליך האינטגרציה של המודם הסלולרי.

The information presented in this document is believed to be accurate and reliable. However, no responsibility is assumed by Telit Communication S.p.A. for its use, nor any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent rights of Telit Communication S.p.A. other than for circuitry embodied in Telit products. This document is subject to change without notice.



**GE863-QUAD
GE863-PY**

1vv0300715 Rev. 1 - 19/09/06

Pin	Signal	I/O	Function	Internal Pull up	Type
59	GPIO17	I/O	GPIO		CMOS 2.8V
60	GPIO14	I/O	GPIO		-
61	RESERVED	-	RESERVED		-
62	RESERVED	-	RESERVED		-
63	DAC_OUT	O	DAC out		
64	GPIO16	I/O	GPIO		CMOS 2.8V
65	RESERVED	-	RESERVED		-
66	RESERVED	-	RESERVED		-
67	GND	-	Ground		Power
68	RESERVED	-	RESERVED		-
69	GND	-	Ground		Power
70	ADC_IN3	AI	Analog / Digital converter input		-
71	GPIO15	I/O	GPIO		-
72	GND	-	Ground		Power
73	RESERVED	-	RESERVED		-
74	ADC_IN2	AI	Analog / Digital converter input		-
75	RESERVED	-	RESERVED	-	-
76	GPIO18	I/O	GPIO		-
77	GND	-	Ground		Power
78	RESERVED	-	RESERVED		-
79	GND	-	Ground		Power
80	RESERVED	-	RESERVED		-

- (1) For the exclusive use of the Technical Support Service
- (2) When activating the Easy camera these pins will not be available for other use
- (3) On this pin a maximum of 10nF bypass capacitor is allowed.
- (4) Available only on GE863-PY




3 Hardware Commands

3.1 Turning ON the GE863-QUAD/PY

To turn on the GE863-QUAD/PY the pad ON# must be tied low for at least 1 second and then released.

The maximum current that can be drained from the ON# pad is 0,1 mA.

A simple circuit to do it is:

 

NOTE: don't use any pull up resistor on the ON# line, it is internally pulled up. Using pull up resistor may bring to latch up problems on the GE863-QUAD/PY power regulator and improper power on/off of the module. The line ON# must be connected only in open collector configuration.

NOTE: In this document all the lines that are inverted, hence have active low signals are labeled with a name that ends with a "#" or with a bar over the name.

NOTE: The GE863-QUAD/PY turns fully on also by supplying power to the Charge pad (provided there's a battery on the VBATT pads).


For example:




**GE863-QUAD
GE863-PY**

1v0300715 Rev. 1 - 19/09/06

 1- Let's assume you need to drive the ON# pad with a totem pole output of a +3/5 V microcontroller (uP_OUT1):



 2- Let's assume you need to drive the ON# pad directly with an ON/OFF button:



3.2 Turning OFF the GE863-QUAD/PY

The turning off of the device can be done in two ways:



- by software command (see GE863-QUAD/PY Software User Guide)
- by hardware shutdown

When the device is shut down by software command or by hardware shutdown, it issues to the network a detach request that informs the network that the device will not be reachable any more.

3.2.1 Hardware shutdown

To turn OFF the GE863-QUAD/PY the pad ON# must be tied low for at least 1 second and then released.

The same circuitry and timing for the power on shall be used.

The device shuts down after the release of the ON# pad.




TIP: To check if the device has powered off, the hardware line PWRCTL should be monitored. When PWRCTL goes low, the device has powered off.

3.3 Hardware Unconditional Reboot

To unconditionally Reboot the GE863-QUAD/PY, the pad RESET# must be tied low for at least 200 milliseconds and then released.

The maximum current that can be drained from the ON# pad is 0,15 mA.

A simple circuit to do it is:

 




NOTE: don't use any pull up resistor on the RESET# line nor any totem pole digital output. Using pull up resistor may bring to latch up problems on the GE863-QUAD/PY power regulator and improper functioning of the module. The line RESET# must be connected only in open collector configuration.



TIP: The unconditional hardware reboot should be always implemented on the boards and software should use it as an emergency exit procedure.

For example:

 1- Let's assume you need to drive the RESET# pad with a totem pole output of a +3/5 V microcontroller (uP_OUT2):



4 Power Supply

The power supply circuitry and board layout are a very important part in the full product design and they strongly reflect on the product overall performances, hence read carefully the requirements and the guidelines that will follow for a proper design.

4.1 Power Supply Requirements

The GE863-QUAD/PY power requirements are:

- *Nominal Supply Voltage:* 3.8 V
- *Max Supply Voltage:* 4.2 V
- *Supply voltage range:* 3.4 V - 4.2 V
- *Max Peak current consumption (impulsive):* 1.9 A
- *Max Average current consumption during GPRS transmission (rms):* 500 mA
- *Max Average current consumption during VOICE/CSD transmission (rms):* 270 mA
- *Average current during Power Saving:* ≈ 4 mA
- *Average current during idle (Power Saving disabled)* ≈ 19 mA

The GSM system is made in a way that the RF transmission is not continuous, else it is packed into bursts at a base frequency of about 216 Hz, the relative current peaks can be as high as about 2A. Therefore the power supply has to be designed in order to withstand with these current peaks without big voltage drops; this means that both the electrical design and the board layout must be designed for this current flow.


If the layout of the PCB is not well designed a strong noise floor is generated on the ground and the supply; this will reflect on all the audio paths producing an audible annoying noise at 216 Hz; if the voltage drop during the peak current absorption is too much, then the device may even shutdown as a consequence of the supply voltage drop.



TIP: The electrical design for the Power supply should be made ensuring it will be capable of a peak current output of at least 2 A.



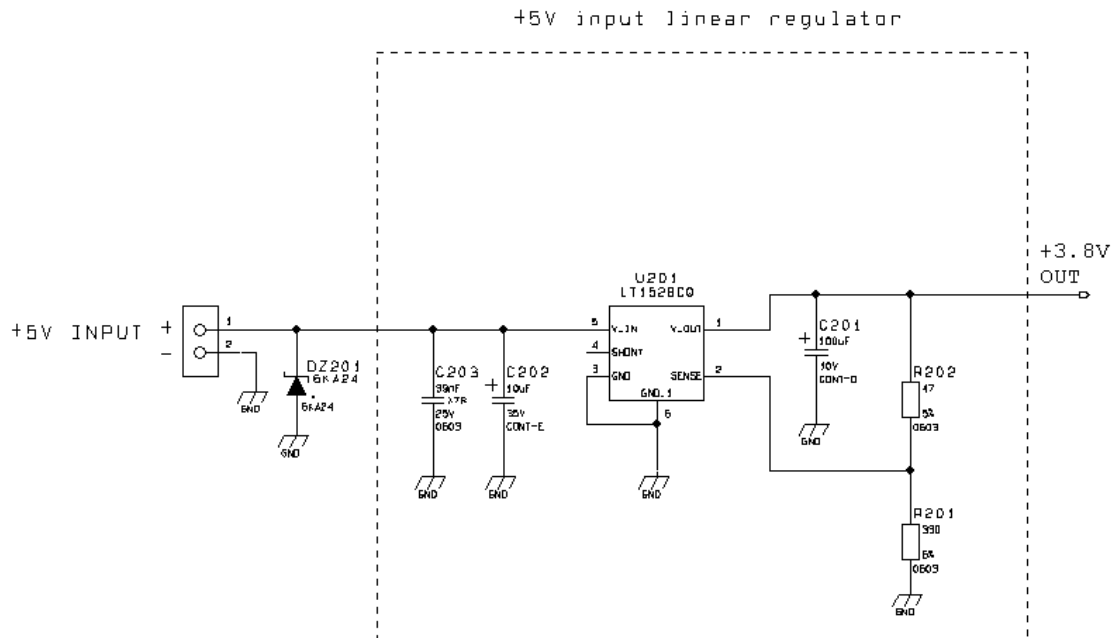An example of linear regulator with 5V input is:




 4.2.1.2 + 12V input Source Power Supply Design Guidelines

- The desired output for the power supply is 3.8V, hence due to the big difference between the input source and the desired output, a linear regulator is not suited and shall not be used. A switching power supply will be preferable because of its better efficiency especially with the 2A peak current load represented by the GE863-QUAD/PY.
- When using a switching regulator, a 500kHz or more switching frequency regulator is preferable because of its smaller inductor size and its faster transient response. This allows the regulator to respond quickly to the current peaks absorption.
- For car PB battery the input voltage can rise up to 15,8V and this should be kept in mind when choosing components: all components in the power supply must withstand this voltage.
- A Bypass low ESR capacitor of adequate capacity must be provided in order to cut the current absorption peaks, a 100µF tantalum capacitor is usually suited.
- Make sure the low ESR capacitor on the power supply output (usually a tantalum one) is rated at least 10V.
- For Car applications a spike protection diode should be inserted close to the power input, in order to clean the supply from spikes.
- A protection diode should be inserted close to the power input, in order to save the GE863-QUAD/PY from power polarity inversion. This can be the same diode as for spike protection.



An example of switching regulator with 12V input is:



4.2.1.3 Battery Source Power Supply Design Guidelines

- The desired nominal output for the power supply is 3.8V and the maximum voltage allowed is 4.2V, hence a single 3.7V Li-Ion cell battery type is suited for supplying the power to the Telit GE863-QUAD/PY module.

The three cells Ni/Cd or Ni/MH 3,6 V Nom. battery types or 4V PB types **MUST NOT BE USED DIRECTLY** since their maximum voltage can rise over the absolute maximum voltage for the GE863-QUAD/PY and damage it.

NOTE: DON'T USE any Ni-Cd, Ni-MH, and Pb battery types directly connected with GE863-QUAD/PY. Their use can lead to overvoltage on the GE863-QUAD/PY and damage it. USE ONLY Li-Ion battery types.

- A Bypass low ESR capacitor of adequate capacity must be provided in order to cut the current absorption peaks, a 100µF tantalum capacitor is usually suited.
- Make sure the low ESR capacitor (usually a tantalum one) is rated at least 10V.
- A protection diode should be inserted close to the power input, in order to save the GE863-QUAD/PY from power polarity inversion. Otherwise the battery connector should be done in a way to avoid polarity inversions when connecting the battery.
- The battery capacity must be at least 500mAh in order to withstand the current peaks of 2A; the suggested capacity is from 500mAh to 1000mAh.



4.2.1.4 Battery Charge control Circuitry Design Guidelines

The charging process for Li-Ion Batteries can be divided into 4 phases:

- Qualification and trickle charging
- Fast charge 1 - constant current
- Final charge - constant voltage or pulsed charging
- Maintenance charge

The qualification process consists in a battery voltage measure, indicating roughly its charge status. If the battery is deeply discharged, that means its voltage is lower than the trickle charging threshold, then the charge must start slowly possibly with a current limited pre-charging process where the current is kept very low with respect to the fast charge value: the trickle charging.

During the trickle charging the voltage across the battery terminals rises; when it reaches the fast charge threshold level the charging process goes into fast charge phase.

During the fast charge phase the process proceeds with a current limited charging; this current limit depends on the required time for the complete charge and from the battery pack capacity. During this phase the voltage across the battery terminals still raises but at a lower rate.

Once the battery voltage reaches its maximum voltage then the process goes into its third state: Final charging. The voltage measure to change the process status into final charge is very important. It must be ensured that the maximum battery voltage is never exceeded, otherwise the battery may be damaged and even explode. Moreover for the constant voltage final chargers, the constant voltage phase (final charge) must not start before the battery voltage has reached its maximum value, otherwise the battery capacity will be highly reduced.

The final charge can be of two different types: constant voltage or pulsed. GE863-QUAD/PY uses constant voltage.

The constant voltage charge proceeds with a fixed voltage regulator (very accurately set to the maximum battery voltage) and hence the current will decrease while the battery is becoming charged. When the charging current falls below a certain fraction of the fast charge current value, then the battery is considered fully charged, the final charge stops and eventually starts the maintenance.

The pulsed charge process has no voltage regulation, instead the charge continues with pulses. Usually the pulse charge works in the following manner: the charge is stopped for some time, let's say few hundreds of ms, then the battery voltage will be measured and when it drops below its maximum value a fixed time length charging pulse is issued. As the battery approaches its full charge the off time will become longer, hence the duty-cycle of the pulses will decrease. The battery is considered fully charged when the pulse duty-cycle is less than a threshold value, typically 10%, the pulse charge stops and eventually the maintenance starts.

The last phase is not properly a charging phase, since the battery at this point is fully charged and the process may stop after the final charge. The maintenance charge provides an additional charging process to compensate for the charge leak typical of a Li-Ion battery. It is done by issuing pulses with a fixed time length, again few hundreds of ms, and a duty-cycle around 5% or less.

This last phase is not implemented in the GE863-QUAD/PY internal charging algorithm, so that the battery once charged is left discharging down to a certain threshold so that it is cycled from full charge to slight discharge even if the battery charger is always inserted. This guarantees that anyway the remaining charge in the battery is a good percentage and that the battery is not damaged by keeping it always fully charged (Li-Ion rechargeable battery usually deteriorate when kept fully charged).

Last but not least, in some applications it is highly desired that the charging process restarts when the battery is discharged and its voltage drops below a certain threshold, GE863-QUAD/PY internal charger does it.



As you can see, the charging process is not a trivial task to be done; moreover all these operations should start only if battery temperature is inside a charging range, usually 5°C - 45°C.

The GE863-QUAD/PY measures the temperature of its internal component, in order to satisfy this last requirement, it's not exactly the same as the battery temperature but in common application the two temperature should not differ too much and the charging temperature range should be guaranteed.

NOTE: For all the threshold voltages, inside the GE863-QUAD/PY all threshold are fixed in order to maximize Li-Ion battery performances and do not need to be changed.

NOTE: In this application the battery charger input current must be limited to less than 400mA. This can be done by using a current limited wall adapter as the power source.

4.2.2 Thermal Design Guidelines

The thermal design for the power supply heat sink should be done with the following specifications:

- Average current consumption during transmission @PWR level max (rms): 500mA
- Average current consumption during transmission @ PWR level min (rms): 100mA
- Average current during Power Saving: 4mA
- Average current during idle (Power Saving disabled) 19mA

NOTE: The average consumption during transmissions depends on the power level at which the device is requested to transmit by the network. The average current consumption hence varies significantly.

Considering the very low current during idle, especially if Power Saving function is enabled, it is possible to consider from the thermal point of view that the device absorbs current significantly only during calls.

If we assume that the device stays into transmission for short periods of time (let's say few minutes) and then remains for a quite long time in idle (let's say one hour), then the power supply has always the time to cool down between the calls and the heat sink could be smaller than the calculated one for 500mA maximum RMS current, or even could be the simple chip package (no heat sink).

Moreover in the average network conditions the device is requested to transmit at a lower power level than the maximum and hence the current consumption will be less than the 500mA, being usually around 150mA.

For these reasons the thermal design is rarely a concern and the simple ground plane where the power supply chip is placed can be enough to ensure a good thermal condition and avoid overheating. For the heat generated by the GE863-QUAD/PY, you can consider it to be during transmission 1W max during CSD/VOICE calls and 2W max during class10 GPRS upload.

This generated heat will be mostly conducted to the ground plane under the GE863-QUAD/PY; you must ensure that your application can dissipate it.



5 Antenna

The antenna connection and board layout design are the most important part in the full product design and they strongly reflect on the product overall performances, hence read carefully and follow the requirements and the guidelines for a proper design.

5.1 GSM Antenna Requirements

As suggested on the Product Description the antenna and antenna line on PCB for a Telit GE863-QUAD/PY device shall fulfil the following requirements:

ANTENNA REQUIREMENTS	
Frequency range	Standard Dual Band GSM/DCS frequency range or Standard Quad Band GSM/DCS/PCS frequency range if used for all four bands
Bandwidth	80 MHz in GSM900, 70MHz in GSM850 & 170 MHz in DCS & 140 MHz PCS band
Gain	Gain < 3dBi
Impedance	50 ohm
Input power	> 2 W peak power
VSWR absolute max	<= 10:1
VSWR recommended	<= 2:1

When using the Telit GE863-QUAD/PY, since there's no antenna connector on the module, the antenna must be connected to the GE863-QUAD/PY through the PCB with the antenna pad.

In the case that the antenna is not directly developed on the same PCB, hence directly connected at the antenna pad of the GE863-QUAD/PY, then a PCB line is needed in order to connect with it or with its connector.

This line of transmission shall fulfil the following requirements:

ANTENNA LINE ON PCB REQUIREMENTS	
Impedance	50 ohm
Max Attenuation	0,3 dB
No coupling with other signals allowed	
Cold End (Ground Plane) of antenna shall be equipotential to the GE863-QUAD/PY ground pins	

Furthermore if the device is developed for the US market and/or Canada market, it shall comply to the FCC and/or IC approval requirements:



**GE863-QUAD
GE863-PY**

1vv0300715 Rev. 1 - 19/09/06

This device is to be used only for mobile and fixed application. The antenna(s) used for this transmitter must be installed to provide a separation distance of at least 20 cm from all persons and must not be co-located or operating in conjunction with any other antenna or transmitter. End-Users must be provided with transmitter operation conditions for satisfying RF exposure compliance. OEM integrators must ensure that the end user has no manual instructions to remove or install the GE863-QUAD/PY module. Antennas used for this OEM module must not exceed 3dBi gain for mobile and fixed operating configurations.

5.2 GSM Antenna - PCB line Guidelines

- Ensure that the antenna line impedance is 50 ohm;
- Keep the antenna line on the PCB as short as possible, since the antenna line loss shall be less than 0,3 dB;
- Antenna line must have uniform characteristics, constant cross section, avoid meanders and abrupt curves;
- Keep, if possible, one layer of the PCB used only for the Ground plane;
- Surround (on the sides, over and under) the antenna line on PCB with Ground, avoid having other signal tracks facing directly the antenna line track;
- The ground around the antenna line on PCB has to be strictly connected to the Ground Plane by placing vias once per 2mm at least;
- Place EM noisy devices as far as possible from GE863-QUAD/PY antenna line;
- Keep the antenna line far away from the GE863-QUAD/PY power supply lines;
- If you have EM noisy devices around the PCB hosting the GE863-QUAD/PY, such as fast switching ICs, take care of the shielding of the antenna line by burying it inside the layers of PCB and surround it with Ground planes, or shield it with a metal frame cover.
- If you don't have EM noisy devices around the PCB of GE863-QUAD/PY, by using a strip-line on the superficial copper layer for the antenna line, the line attenuation will be lower than a buried one;

5.3 GSM Antenna - installation Guidelines

- Install the antenna in a place covered by the GSM signal.
- The Antenna must be installed to provide a separation distance of at least 20 cm from all persons and must not be co-located or operating in conjunction with any other antenna or transmitter;
- Antenna shall not be installed inside metal cases
- Antenna shall be installed also according Antenna manufacturer instructions.

6 Serial Ports

The serial port on the Telit GE863-QUAD/PY is the core of the interface between the module and OEM hardware.

2 serial ports are available on the module:



- MODEM SERIAL PORT
- MODEM SERIAL PORT 2 (DEBUG)

6.1 MODEM SERIAL PORT

Several configurations can be designed for the serial port on the OEM hardware, but the most common are:

- RS232 PC com port
- microcontroller UART @ 2.8V - 3V (Universal Asynchronous Receive Transmit)
- microcontroller UART@ 5V or other voltages different from 2.8V

Depending from the type of serial port on the OEM hardware a level translator circuit may be needed to make the system work. The only configuration that doesn't need a level translation is the 2.8V UART.

The serial port on the GE863-QUAD/PY is a +2.8V UART with all the 7 RS232 signals. It differs from the PC-RS232 in the signal polarity (RS232 is reversed) and levels. The levels for the GE863-QUAD/PY UART are the CMOS levels:

Absolute Maximum Ratings -Not Functional

Parameter	Min	Max
Input level on any digital pad when on	-0.3V	+3.75V
Input voltage on analog pads when on	-0.3V	+3.0 V

Operating Range - Interface levels (2.8V CMOS)

Level	Min	Max
Input high level V_{IH}	2.1V	3.3V
Input low level V_{IL}	0V	0.5V
Output high level V_{OH}	2.2V	3.0V
Output low level V_{OL}	0V	0.35V



**GE863-QUAD
GE863-PY**

1vv0300715 Rev. 1 - 19/09/06

The signals of the GE863-QUAD/PY serial port are:

RS232 Pin Number	Signal	GE863-QUAD/PY Pad Number	Name	Usage
1	DCD - dcd_uart	42	Data Carrier Detect	Output from the GE863-QUAD/PY that indicates the carrier presence
2	RXD - tx_uart	38	Transmit line *see Note	Output transmit line of GE863-QUAD/PY UART
3	TXD - rx_uart	37	Receive line *see Note	Input receive of the GE863-QUAD/PY UART
4	DTR - dtr_uart	39	Data Terminal Ready	Input to the GE863-QUAD/PY that controls the DTE READY condition
5	GND	8-17-28-36-45-48-50-56	Ground	ground
6	DSR - dsr_uart	43	Data Set Ready	Output from the GE863-QUAD/PY that indicates the module is ready
7	RTS - rts_uart	40	Request to Send	Input to the GE863-QUAD/PY that controls the Hardware flow control
8	CTS - cts_uart	41	Clear to Send	Output from the GE863-QUAD/PY that controls the Hardware flow control
9	RI - ri_uart	44	Ring Indicator	Output from the GE863-QUAD/PY that indicates the incoming call condition

NOTE: According to V.24, RX/TX signal names are referred to the application side, therefore on the GE863-QUAD/PY side these signal are on the opposite direction: TXD on the application side will be connected to the receive line (here named TXD/ rx_uart) of the GE863-QUAD/PY serial port and viceversa for RX.

TIP: For a minimum implementation, only the TXD and RXD lines can be connected, the other lines can be left open provided a software flow control is implemented.

The signals in the UART connector on the EVK are:

DCD	RXD
TXD	DTR
GND	DSR
RTS	CTS
RI	GND




**GE863-QUAD
GE863-PY**


1v0300715 Rev. 1 - 19/09/06

NOTE: In order to be able to do in circuit reprogramming of the GE863-QUAD/PY firmware, the serial port on the Telit GE863-QUAD/PY shall be available for translation into RS232 and either it's controlling device shall be placed into tristate, disconnected or as a gateway for the serial data when module reprogramming occurs. Only RXD, TXD, GND and the On/off module turn on pad are required to the reprogramming of the module, the other lines are unused. All applicator shall include in their design such a way of reprogramming the GE863-QUAD/PY.

 An example of level translation circuitry of this kind is:




 The RS232 serial port lines are usually connected to a DB9 connector with the following layout:




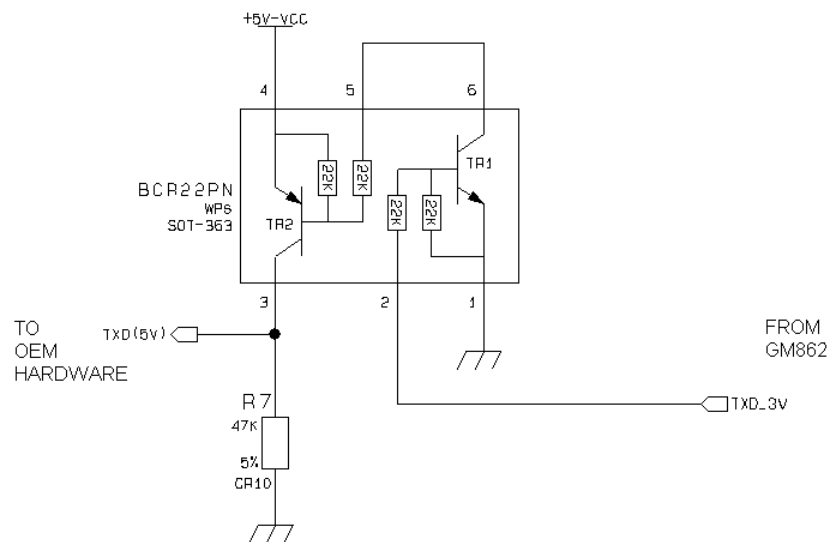6.4 5V UART level translation

If the OEM application uses a microcontroller with a serial port (UART) that works at a voltage different from 2.8 - 3V, then a circuitry has to be provided to adapt the different levels of the two set of signals. As for the RS232 translation there are a multitude of single chip translators, but since the translation requires very few components, then also a discrete design can be suited. For example a possible inexpensive translator circuit for a 5V driver can be:



and for a 5V receiver:

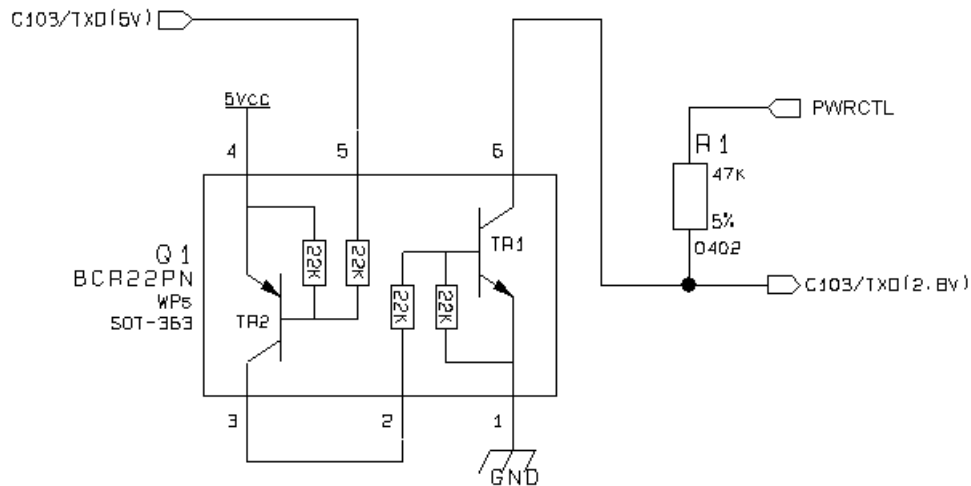

NOTE: The UART input line TXD (rx_uart) of the GE863-QUAD/PY is NOT internally pulled up with a resistor, so there may be the need to place an external 47KΩ pull-up resistor, either the DTR (dtr_uart) and RTS (rts_uart) input lines are not pulled up internally, so an external pull-up resistor of 47KΩ may be required.

A power source of the internal interface voltage corresponding to the 2.8VCMOS high level is available at the VAUX pad, whose absolute maximum output current is 100mA.

If VAUX is also used to supply a Camera no additional devices could be connected.

Pull-up resistors can be connected to the VAUX pad provided that the pulled-up lines are GE863-QUAD/PY input lines connected to open collector outputs in order to avoid latch-up problems on the GE863-QUAD/PY.

Care must be taken to avoid latch-up on the GE863-QUAD/PY and the use of this output line to power electronic devices shall be considered with care, especially for devices that generate spikes and noise such as level translators, digital ICs or microcontroller, failure in any of these condition can severely compromise the GE863-QUAD/PY functionality.



NOTE: The input lines working at 2.8VCMOS can be pulled-up with 47KΩ resistors that can be connected directly to the VAUX line.

NO disturbing devices should be powered with the VAUX line; otherwise the module functionality may be compromised.



7 Audio Section Overview

The Base Band Chip of the GE863-QUAD / PY Telit Module provides two different audio blocks; both in transmit (*Uplink*) and in receive (*Downlink*) direction:

“*MT lines*” should be used for handset function,
“*HF lines*” is suited for hands -free function (car kit).


These two blocks can be active only one at a time, selectable by *AXE* hardware line or by AT command.

The audio characteristics are equivalent in transmit blocks, but are different in the receive ones and this should be kept in mind when designing.



GE863-QUAD
GE863-PY

1v0300715 Rev. 1 - 19/09/06

 

7.1 Microphone Paths Characteristic and Requirements



TIP: being the microphone circuitry the more noise sensitive , its design and layout must be done with particular care. Both microphone paths are balanced and the OEM circuitry should be balanced designed to reduce the common mode noise typically generated on the ground plane. However also an unbalanced circuitry can be used for particular OEM application needs



*TIP: due to the difference in the echo canceller type, the “Mic_MT” audio path is suited for Handset applications, while the “Mic_HF” audio path is suited for hands-free function (car kit). The Earphone applications should be made using the “Mic_HF” audio path but **DISABLING** the echo canceller by software AT command. If the echo canceller is left active with the Earphone, then some echo might be introduced by the echo cancel algorithm.*

“Mic_MT” 1st differential microphone path

<ul style="list-style-type: none"> • line coupling • line type • coupling capacitor • differential input resistance • differential input voltage • microphone nominal sensitivity • analog gain suggested • echo canceller type 	<p>AC balanced $\geq 100\text{nF}$ $50\text{k}\Omega$ $\leq 1,03\text{V}_{\text{pp}}$ ($365\text{mV}_{\text{rms}}$) $-45 \text{ dBV}_{\text{rms}}/\text{Pa}$ $+ 20\text{dB}$ handset</p>
---	--

“Mic_HF” 2nd differential microphone path

<ul style="list-style-type: none"> • line coupling • line type • coupling capacitor • differential input resistance • differential input voltage • microphone nominal sensitivity • analog gain suggested • echo canceller type 	<p>AC balanced $\geq 100\text{nF}$ $50\text{k}\Omega$ $\leq 65\text{mV}_{\text{pp}}$ (23mV_{rms}) $-45 \text{ dBV}_{\text{rms}}/\text{Pa}$ $+10\text{dB}$ car kit hands-free</p>
---	--





TIP: definition of the nominal sensitivity of the microphone lines .

The nominal sensitivity of the microphone lines indicates the voltage level on the GE863-QUAD / PY pins present during "normal spoken" conditions.
For a handset , the "normal spoken" conditions take place when the talker mouth is 7cm far from the microphone ; under these conditions the voice will produce an acoustic pressure of $-4,7\text{dBPa} @ 1\text{kHz}$ on the microphone membrane .



TIP: electrical equivalent signal and operating voice levels .

At "normal spoken" conditions, a microphone having the suggested nominal sensitivity of $-45\text{dBV}_{\text{rms}}/\text{Pa}$, will produce

the electrical equivalent signal :

$$\text{MicLevel} = (-45) + (-4.7) = -49.7 \text{ dB}_{\text{Vrms}}$$

that means :

$$\text{MicVoltage} = 10^{(-49.7/20)} = 3.3 * 10^{-3} \text{ V}_{\text{rms}}$$

During a call, this level varies according to the volume of the talker voice; usually the following rough thumb rule for the dynamic range may be used :

- 1) the talker is screaming . This is the *strongest voice level* condition: the signal increases by +20dB;
- 2) the talker is whispering. This is the *lowest voice level* condition: the voice level decreases by – 50dB.

These changes must be considered for designing the external microphone amplifier.



TIP: example of external microphone amplifier calculation .

Let's suppose to use the *1st differential* microphone path .In this case the maximum differential input voltage to "Mic_MT" lines is $365\text{mV}_{\text{rms}}(1,03\text{V}_{\text{pp}})$ corresponding to $-8,76\text{dBV}$.

Now we can calculate the maximum voltage gain of an external microphone amplifier G_A :

$$[(\text{MicLevel} + 20\text{dB}) + G_A] = -8,76\text{dBV}$$

$$[-49,7 + 20 + G_A] = -8,76$$

$$-40,9 + 20 = -G_A$$

$$G_A = 20,94\text{dB}$$

→ you can set $G_A = +20\text{dB}$ to use standard resistor values .




7.4 Microphone Biasing

The electret microphones usually need a biasing voltage to work properly. Refer to your microphone provider for the characteristics required.

NOTE: *The microphones have a hot wire were the positive biasing must be connected. Usually it is indicated by a + symbol or a red point. If the polarity of the bias is reversed, then the microphone will not work properly. For this reason be sure to respect the mic. biasing polarity.*

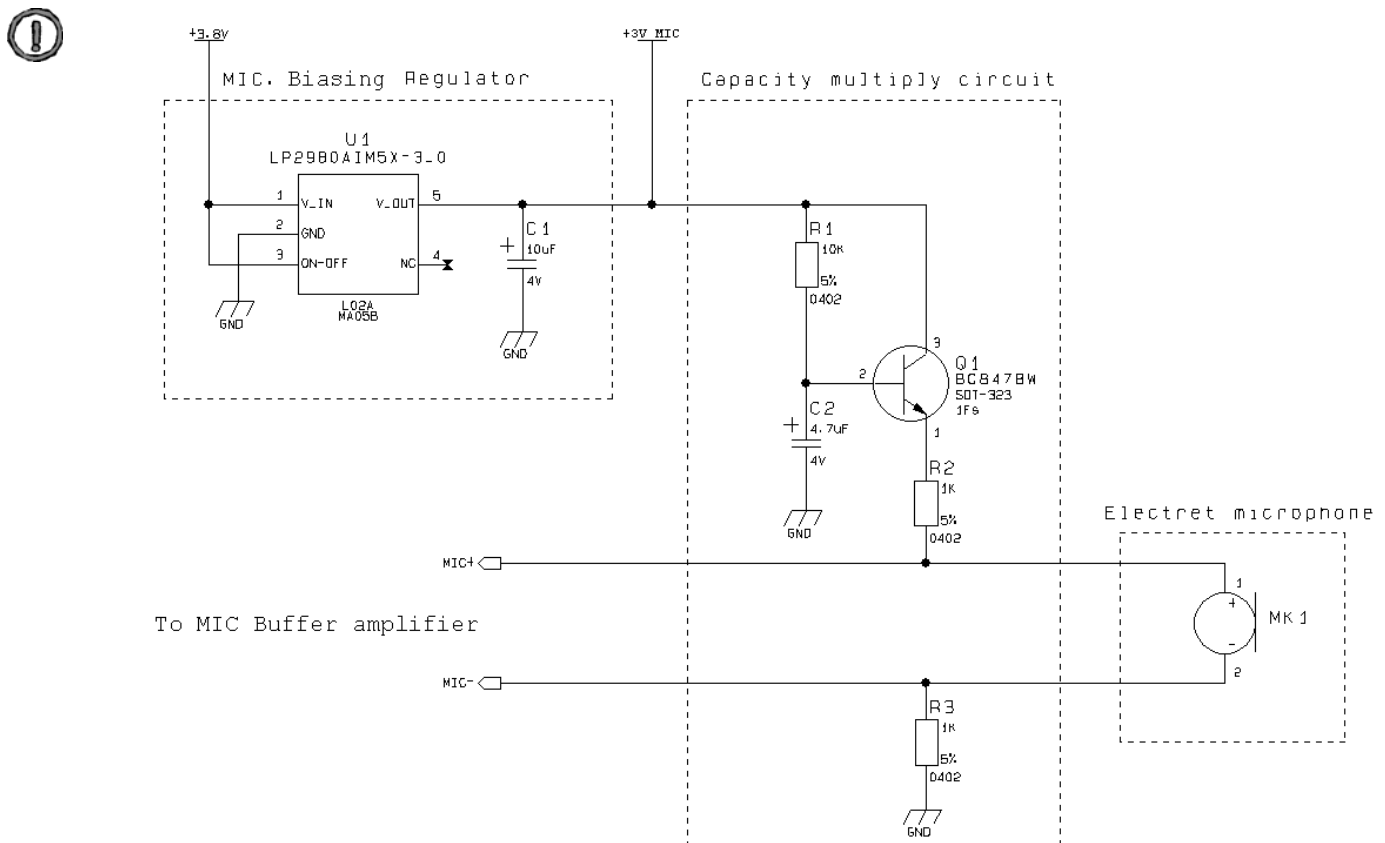7.4.1 Balanced Microphone Biasing

The balanced microphone bias voltage should be obtained from a dedicated voltage regulator, in order to eliminate the noise present on the power lines. This regulator can be the same for all the audio paths. The microphone should be supplied from a capacitor multiply circuit. For example a circuit for the balanced microphone biasing can be:



NOTE: *In the balanced application the resistors R2 and R3 must have the same value to keep the circuit balanced.*




NOTE: The cable to the microphone should not be shielded, instead a twisted pair cable shall be used.


NOTE: The microphone sensitivity changes with the value of R2 and R3. Usually the microphones are characterized with 2kΩ biasing resistance, so try to keep the sum of R2 and R3 around 2kΩ. Refer to your microphone manufacturer for the mic. characteristics.

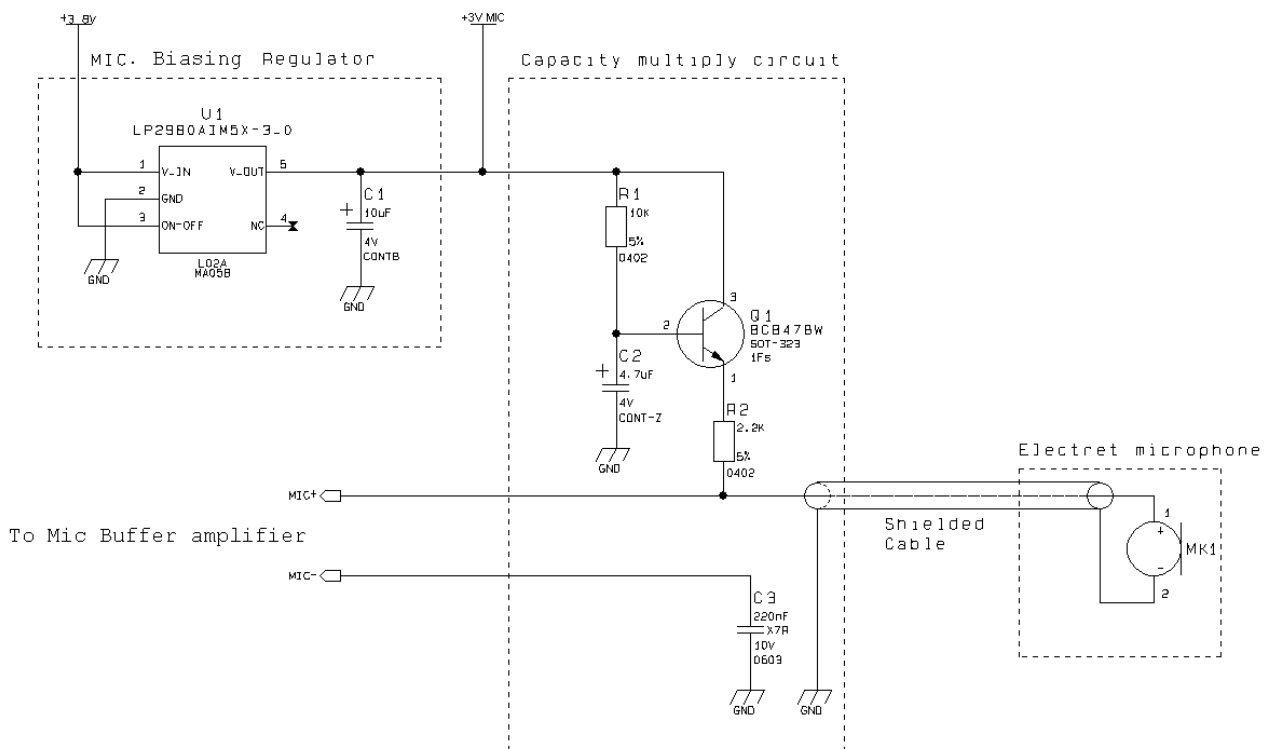7.4.2 Unbalanced Microphone Biasing

The unbalanced microphone biasing voltage should be obtained from a dedicated voltage regulator, in order to eliminate the noise present on the power lines. This regulator can be the same for all the audio paths. The microphone should be supplied from a capacitor multiply circuit. For example a circuit for the unbalanced microphone biasing can be:



 7.5.2 Buffered Unbalanced (Single Ended) Microphone .



The above schematic can be used for a single ended (*buffered unbalanced*) microphone ; the required biasing circuitry is not included. Note also that the capacitor C3 is not needed .
The gains of the two amplifiers are given by the formulas :

$$Gain(\text{not inverting buffer}) = 1 + \frac{R719}{R720} \qquad Gain(\text{inverting buffer}) = \frac{R718}{R720}$$

Assigning half of overall gain to each amplifier, you will obtain the requested gain because of doubling the microphone signal path; in fact by the use of two amplifiers (the upper as “inverting” and the lower as “not inverting” configuration) we obtain an additional +6dB gain (2 times) .

Remember : the “not inverting “ amplifier section gain shall not be less than 1 .

Like for the balanced buffered microphone , the amplifier overall gain can be modify changing the value of resistor R719/R720 and R718 and as a consequence the capacitors C726 and C727. It is advisable to change R708 only if you have difficulty to find a commercial value for R711 ; in this case change R708 as little as possible .

The -3dB bandwidth is given by the approximated formula (considering C725 >> C726):



$$freq. = \frac{1}{2\pi * R719 * C726} = \frac{1}{2\pi * R711 * C727} \text{ [Hz]}$$

The buffer bandwidth at -3dB shall be 4KHz.

Note that the biasing of the operational amplifier is given for the inverting amplifier by the series divider R714-R715. The 100nF capacitor C719 is needed to filter the noise that could be coupled to that divider. For the not inverting operational amplifier the biasing is given by a different divider R715-R717 with the capacitor C720 and through a series resistor R718 of 470KΩ.



TIP: example of calculation.

Let's assume you have a microphone with a sensitivity of $-45\text{dBV}_{\text{rms}}/\text{Pa}$ and you want to use it in 2nd differential microphone path ("Mic_HF" inputs) in "normal spoken" conditions at acoustic pressure of -4.7dBPa .

As reported at page XX, the electrical level output from the microphone will be :

$$\text{MicLevel} = (-45) + (-4.7) = -49.7 \text{ dBV}_{\text{rms}}$$

but we have to consider 20dB loss due to the higher distance from the mouth of the talker (50cm) .

$$\text{MicLevel} = (-49.7) + (-20) = -69.7 \text{ dBV}_{\text{rms}}$$

corresponding to

$$\text{MicVoltage} = 10^{(-69.7 / 20)} = 0,33 * 10^{-3}$$

In order to have a signal of $1 \text{ mV}_{\text{rms}}$ at the "Mic_HF" inputs, as suggested at TIP "environment consideration",

the buffer must have a gain

$$G_A = \text{Mic_HF} / \text{MicVoltage} = (1 * 10^{-3}) / (0,33 * 10^{-3}) = 3 \quad \text{or } +10 \text{ dB}$$

Keeping in mind that "balancing the line will double the signal", to calculate the resistor values assign half of required gain G_A to each amplifier section. And therefore $G_S = 1,5$ times (or +3,52dB).

Choosing as $10\text{k}\Omega$ as the input resistance, the corresponding values for the resistors on the buffer will be :

$$R711 = G_S * R708 = 1.5 * 10 = 15 \text{ k}\Omega$$

$$R719 = (G_S - 1) * R720 = (1.5 - 1) * 10 = 5 \text{ k}\Omega$$

The commercial values of $15\text{k}\Omega$ and $5.6\text{k}\Omega$ be accepted.



GE863-QUAD
GE863-PY

1vv0300715 Rev. 1 - 19/09/06

As a consequence of the assigned values of the resistors, the nominal values of C726 and C727 are :

$$C726 = 1 / (2\pi * 4000 * R719) = 7.10 * 10^{-9} F$$

$$C727 = 1 / (2\pi * 4000 * R711) = 2,65 * 10^{-9} F$$

*modified in **6,8nF** ($f_{c1}=4181\text{Hz}$) and **2,7nF** ($f_{c2}=3931\text{Hz}$) because of commercial values .*



8.2 Output Lines Characteristics

“Ear_MT” Differential Line-out Drivers Path

- | | |
|------------------------------------|---|
| • line coupling: | DC |
| • line type: | bridged |
| • output load resistance : | $\geq 14 \Omega$ |
| • internal output resistance: | 4 Ω (typical) |
| • signal bandwidth: | 150 - 4000 Hz @ -3 dB |
| • max. differential output voltage | 1310 mV _{rms} (typ, open circuit) |
| • differential output voltage | 328mV _{rms} /16 Ω @ -12dBFS |
| • SW volume level step | - 2 dB |
| • number of SW volume steps | 10 |

“Ear_HF” Power Buffers path

- | | |
|------------------------------------|--|
| • line coupling: | DC |
| • line type: | bridged |
| • output load resistance : | $\geq 14 \Omega$ |
| • internal output resistance: | 4 Ω (>1,7 Ω) |
| • signal bandwidth: | 150 - 4000 Hz @ -3 dB |
| • max. differential output voltage | 1310 mV _{rms} (typ, open circuit) |
| • max. single ended output voltage | 656 mV _{rms} (typ, open circuit) |
| • SW volume level step | - 2 dB |
| • number of SW volume steps | 10 |



8.3 General Design Rules

There are several configurations for the audio output path, but the various design requirements can be grouped into three different categories:

- handset earphone (low power, typically a handset)
- hands-free earphone (low power, typically a earphone)
- car kit speakerphone (high power, typically a speaker)

The three groups have different power requirements, usually the first two applications need only few mW of power, which can be directly drained from the GE863-QUAD / PY pads, provided a suited speaker is used. This direct connect design is the cheaper and simpler solution and will be suited for the most of the earphone design requirements. There's no need to decouple the output ear lines if a suited earpiece is connected. For the last group, the speakerphone, a power amplifier is required to raise the output power up to 5-10W required in a car cabin application.

All the designs shall comply with the following guidelines:

- Where possible use a bridged earphone circuitry, to achieve the maximum power output from the device.
- Keep the earphone traces on the PCB and wires as short as possible.
- If your application requires a single ended earpiece and you want a direct connection, then leave one of the two output lines open and use only the other referred to ground. Remember that in this case the power output is 4 times lower than the bridged circuit and may not be enough to ensure a good voice volume.
- Make sure that the earphone traces in the PCB don't cross or run parallel to noisy traces (especially the power line)
- The cable to the speaker shall be a twisted pair with both the lines floating for the bridged output type, shielded with the shield to ground for the single ended output type.

8.3.1 Noise Filtering

The I/O of the PCB should have a noise filter close to the connector, to filter the high frequency GSM noise. The filter can be a Π formed by 2 capacitor and a inductance, with the one capacitor of $39pF - 0603$ case , and the other capacitor of $1nF - 0603$; the inductance shall have a value of $39\mu H$.




The resulting gain and high pass cut can be obtained with the formula:

$$Gain = \frac{R3}{R2}$$

$$freq. = \frac{1}{2\pi * R3 * C4} \text{ [Hz]}$$

 And an example of internal Ear amplifier could be :



Some amplifier require a low impedance load at high frequency in order to avoid auto oscillation, this can be made with a capacitor (100nF) in series with a resistor (15Ω).

When designing your application, remember to provide an adequate bypass capacitor to the amplifier and place it close to the power input pin of the IC, keeping the traces as short as possible.

8.5 Hands-Free Earphone (Low Power) Design

The same design considerations made for the handset are valid for the hands-free earphone.



8.6 Car Kit Speakerphone Design


For the car kit speaker phone function the power output requirement is usually at least 4W, therefore an amplifier is needed to boost the *GE863-QUAD / PY* output.

The design of the amplifier shall comply with the following guidelines:

- The input to the amplifier **MUST** be taken from the “*Ear_HF*” audio path of the *GE863-QUAD / PY*, because of its echo canceller parameters suited to a car cabin use.
- The amplifier shall have a gain of 30-40 times (29-32 dB) to provide the desired output power of 5-10W with the signal from the *GE863-QUAD / PY* “*Ear_HF*” audio output lines.
- If the amplifier has a fixed gain then it can be adjusted to the desired value by reducing the input signal with a resistor divider network.
- The amplifier shall have a mute control to be used while not in conversation. This results in two benefits: eliminating the background noise when not in conversation and saving power.
- The power to the amplifier should be decoupled as much as possible from the *GE863-QUAD / PY* power supply, by either keeping separate wires and placing bypass capacitors of adequate value close to the amplifier power input pads.
- The biasing voltage of the amplifier shall be stabilized with a low ESR (e.g. a tantalum) capacitor of adequate value.

NOTE: The *GE863-QUAD / PY* audio path connected to the car kit hands-free amplifier **MUST** be “*Ear_HF*” one, otherwise the echo cancellation will not be done due to the difference in the echo canceller characteristics of the *GE863-QUAD / PY* internal audio path from the external audio path.

Example of car kit amplifier schematic.

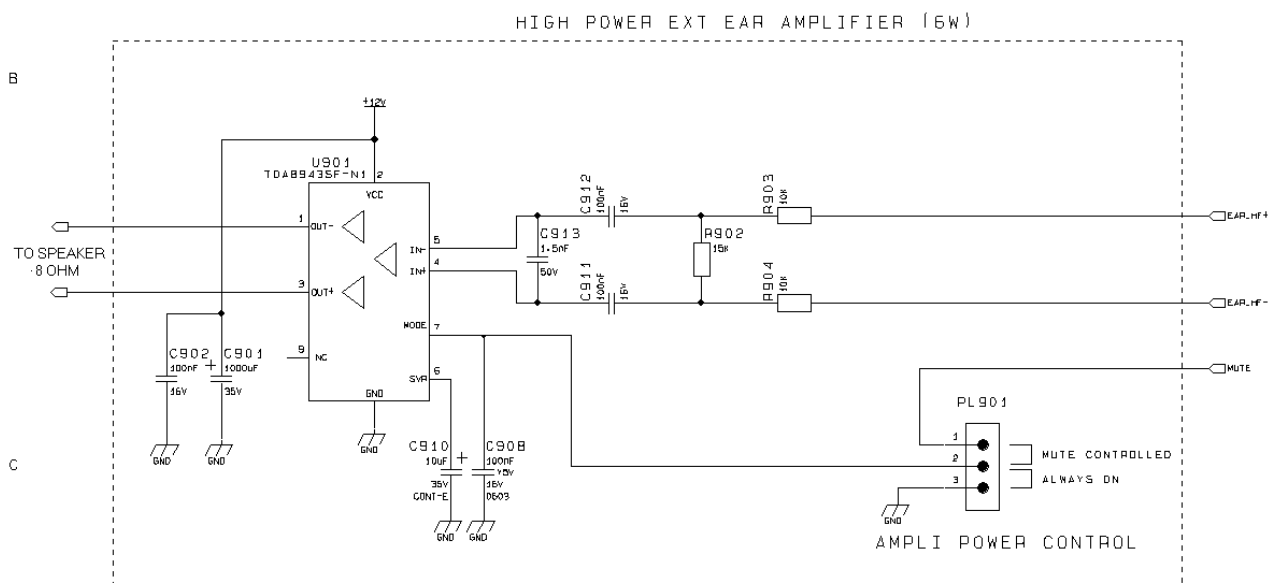

The ASC1 port is used for:

- Continuous of debug messages of the PYTHON Script Interpreter (requires PYTHON version modules;

For further detailed description refer to Technical Specification 30276st10285a_r3.

8.7.2 EVK2 Audio Lines Characteristics

Low Power Audio1 Outputs (*Ear_MT+” line*)

- | | |
|--|--|
| <ul style="list-style-type: none"> • line coupling: • line type: • load impedance: • signal bandwidth: • max.output • max. differential output voltage | <p>AC</p> <p>single ended referred to GND</p> <p>$\geq 16 \Omega$</p> <p>150 - 4000 Hz @ -3 dB</p> <p>655mV_{rms} (open circuit)</p> <p>164mV_{rms} (typ) /16 Ω @ -12dBFS</p> |
|--|--|

Low Power Audio2 Outputs (*Ear_HF+” line*)

- | | |
|--|---|
| <ul style="list-style-type: none"> • line coupling: • line type: • load impedance: • signal bandwidth: • max. single ended output voltage | <p>AC</p> <p>single ended referred to GND</p> <p>$\geq 16 \Omega$</p> <p>150 - 4000 Hz @ -3 dB</p> <p>655mV_{rms} (open circuit)</p> |
|--|---|

High Power Audio1 / Audio2 Outputs

- | | |
|--|--|
| <ul style="list-style-type: none"> • line coupling: • line type: • load impedance: • signal bandwidth: • maximum power output: • THD+N | <p>DC</p> <p>balanced</p> <p>$\geq 8 \Omega$</p> <p>150 - 4000 Hz @ -3 dB</p> <p>500 mW @ 8 Ω</p> <p>1% @ 350mW</p> |
|--|--|



9 SIM DESIGN GUIDES

In all Telit modules there are five pins for SIM card holder connection
These lines are:

SIMVCC	(SIM Power supply)
SIMRST	(SIM Reset)
SIMIO	(SIM Data)
SIMIN	(SIM Presence/Absence)
SIMCLK	(SIM Clock)

SIM connection must take in account of **four** key issues:

9.1 Data Integrity

Standard rules for digital layout and routing must be followed taking in consideration that SIMCLK has frequency of 3.57 MHz and SIMIO has 9600Bps baud rate.

9.2 EMI/EMC

This is a key aspect to consider designing an application based on TELIT module with internal antenna and/or without a proper-shielded box. Some of these conditions may occur:

- Antenna picks-up digital noise coming from SIM card lines.
- Antenna radiated field may interfere digital lines.
- Digital lines (in particular clock) may radiate spurious in the surrounding space.

To overcome all these potential problems, connection lines must be kept as short as possible and shielded.

SIM-holder position has to be as far as possible from antenna.

RF bypass capacitors (10pF...33pF) closed to SIM card SIM-holder are another good care.

When connection is not short, insertion of 10..100ohm resistor with 10..33pF capacitor (RC filter) is a good caution to improve EMI from SIMCLK line.

Do not insert resistor on SIMVCC, SIMRST and SIMIO lines, their use is not supported by SIM electrical interface.

9.3 ESD

Take standard ESD caution if application based on TELIT module has SIM holder with contacts reachable from human body.




9.4 SIM Supply

Do not connect capacitance greater than 10nF to SIMVCC line.


Other notes:

- SIMIN doesn't require any pull-up resistor. It is built in.
- SIM card is detected inserted when this line is short to ground.
- If in the application the SIM holder doesn't foresee the switch for the presence/absence of the SIM card, the **SIMIN** line must be connected to ground.

9.5 SCHEMATIC

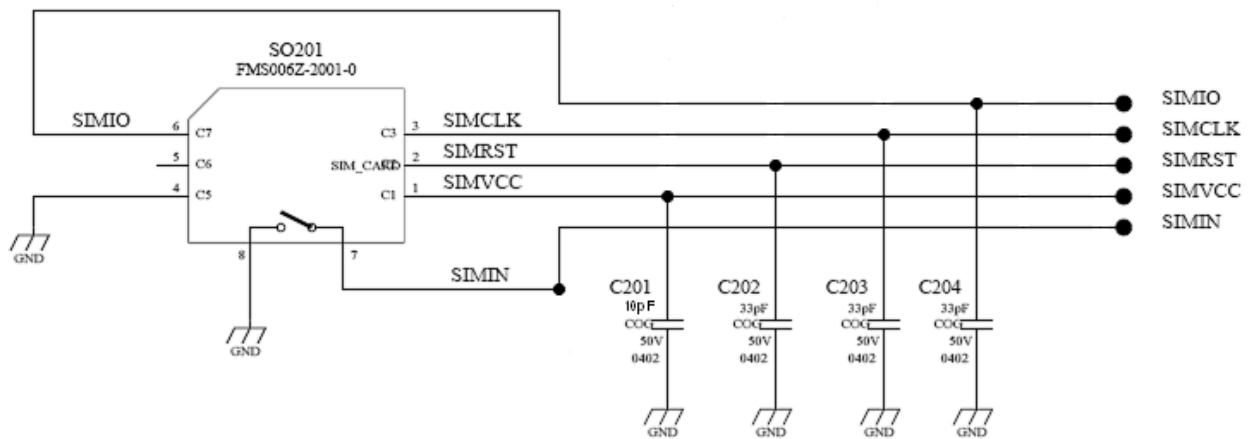

9.6 LAYOUT

 

10 General Purpose I/O

The general purpose I/O pads can be configured to act in three different ways:

- input
- output
- alternate function (internally controlled)

Input pads can only be read and report the digital value (high or low) present on the pad at the read time; output pads can only be written or queried and set the value of the pad output; an alternate function pad is internally controlled by the GE863-QUAD / PY firmware and acts depending on the function implemented.

Not all GPIO pads support all these three modes:

- GPIO5 supports all three modes and can be input, output, RFTX monitor output (Alternate function)
- GPIO6 supports all three modes and can be input, output, alarm output (Alternate function)
- GPIO7 supports all three modes and can be input, output, buzzer output (Alternate function)

All GPIO pads are 2.8V CMOS signals and their interface levels are the same specified in the paragraph 5 .

10.1 Using a GPIO Pad as INPUT

The GPIO pads, when used as inputs, can be connected to a digital output of another device and report its status, provided this device has interface levels compatible with the 2.8V CMOS levels of the GPIO.

If the digital output of the device to be connected with the GPIO input pad has interface levels different from the 2.8V CMOS, then it can be connected to GPIO1 or can be buffered with an open collector transistor, provided a 47KΩ pull-up resistor is connected as seen in the paragraph 6.4 5V UART level translation.

10.2 Using a GPIO Pad as OUTPUT

The GPIO pads, when used as outputs, can drive 2.8V CMOS digital devices or compatible hardware. When set as outputs, the pads have a push-pull output and therefore the pull-up resistor may be omitted.



10.3 Using the Alarm Output GPIO6

The GPIO6 pad, when configured as Alarm Output, is controlled by the GE863-QUAD / PY module and will rise when the alarm starts and fall after the issue of a dedicated AT command.


This output can be used to power up the GE863-QUAD / PY controlling microcontroller or application at the alarm time, giving you the possibility to program a timely system wake-up to achieve some periodic actions and completely turn off either the application and the GE863-QUAD / PY during sleep periods, dramatically reducing the sleep consumption to few μA .

In battery powered devices this feature will greatly improve the autonomy of the device.

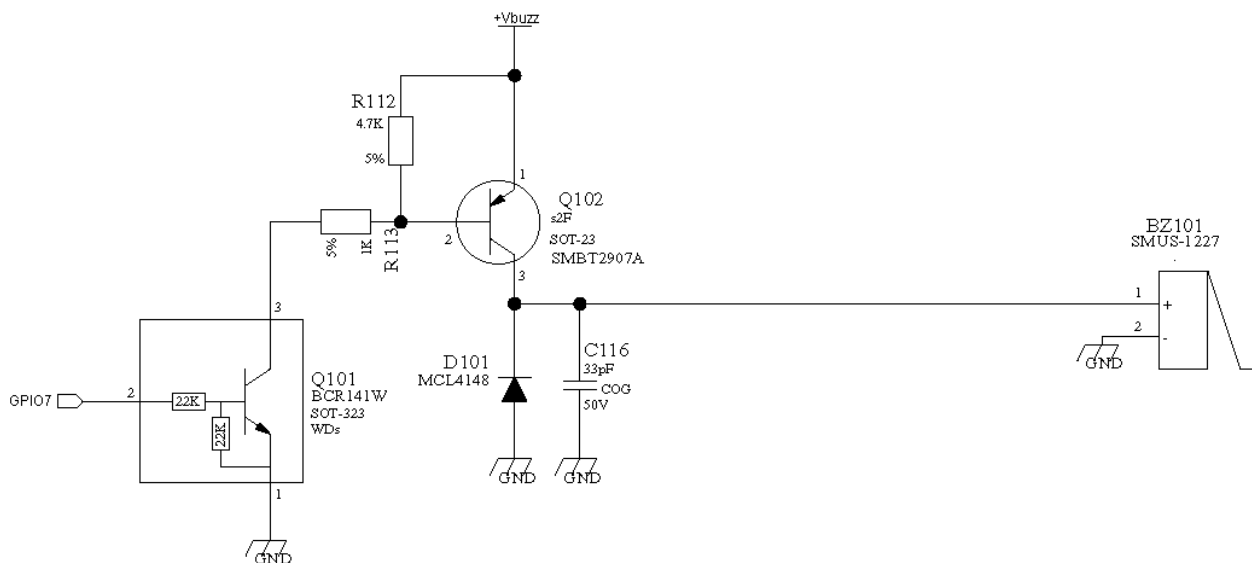10.4 Using the Buzzer Output GPIO7

The GPIO7 pad, when configured as Buzzer Output, is controlled by the GE863-QUAD / PY module and will drive with appropriate square waves a Buzzer driver.

This permits to your application to easily implement Buzzer feature with ringing tones or melody played at the call incoming, tone playing on SMS incoming or simply playing a tone or melody when needed by your application.



A sample interface scheme is included below to give you an idea of how to interface a Buzzer to the GPIO7:



NOTE: To correctly drive a buzzer a driver must be provided, its characteristics depend on the Buzzer and for them refer to your buzzer vendor.



11.1.2 Enabling DAC

An AT command is available to use the DAC function.


The command is **AT#DAC[=<enable>[,<value>]]**

<value> - scale factor of the integrated output voltage (0..1023 - 10 bit precision)
it must be present if **<enable>=1**

Refer to SW user guide or to GE863-QUAD / PY AT commands specification for the full description of this function.

 **NOTE: The DAC frequency is selected internally. D/A converter must not be used during POWERSAVING.**

11.1.3 Low Pass Filter Example

 

12.1.1 Camera Interface Connectors

The pinout of the module and a 24 pins ZIF connector for the CMOS camera provide the interface connection between GE863-QUAD / PY and Transchip camera.

GE863-QUAD / PY signal			Notes	TC5747MF24L		
Pin	Signal	I/O		Pin	Signal	I/O
55	GPIO3	O	I2C bus serial clock	1	SCLK	I
8-17...	GND		Ground	2	AGND	I
31	VAUX	O	Power Supply	3	AVDD28*	I
5	GPIO9	O	Camera Reset	4	RESET_N	I
7	MON1_CAM	O	Clock	5	CLK_IN**	I
8-17...	GND		Ground	6	DGND	I
	n.c		n.c.	7	DOUT_0	I/O
	n.c		n.c.	8	DOUT_1	I/O
	n.c		n.c.	9	DOUT_2	I/O
	n.c		n.c.	10	DOUT_3	I/O
	n.c		n.c.	11	DOUT_4	I/O
	n.c		n.c.	12	DOUT_5	I/O
	n.c		n.c.	13	DOUT_6	I/O
	n.c		n.c.	14	DOUT_7	I/O
	n.c		n.c.	15	DOUT_8	I/O
	n.c		n.c.	16	VCLKOUT	O
	n.c		n.c.	17	VALIDH	O
	n.c		n.c.	18	VALIDV	O
31	VAUX	O	Power Supply	19	DVDD28	I
32	GPIO4	I/O	I2C bus serial data	20	SDIN	I/O
8-17..	GND		Ground	21	PS1	I
6	GPIO8	O	Camera power type selector	22	PS2	I
8-17...	GND		Ground	23	SHIELD	-
			Flash Enable	24	LED_CTRL	O

Filter the AVDD28.

** Use a Buffer between module clk out, MON1_CAM and camera clk in, CLK_IN.


*** Non-connected.



 12.1.2 EVB for Transchip camera support


In order to interface the Telit GE863-QUAD / PY with a CMOS camera, Telit has developed an evaluation board. The EVK allows the connector of all Telit modules through 2 connectors of 40 pins each.

The I2CBUS DUAL CAMERA board is plugged in the 2 connectors of 30 pins each on the module board.



 12.1.3 Block Diagram for supported cameras

The numbers on the left side of the Camera's connectors refers to Module Connector's pin number.
DVDD is VAUX1 power supply from GE863-QUAD / PY



12.1.5 Example usage script for camera

Camera setting: (shown here are the defaults ones)

>AT#CAMSEL=0	(camera selection: 0-auto, 1-agilent, 2-transchip)
OK	
>AT#CMODE=0	(camera mode: 0-day, 1-night)
OK	
>AT#CAMQUA=0	(camera quality: 0-low, 1-medieum, 2-high)
OK	
>AT#CAMRES=0	(camera resolution: 0-VGA, 1-QVGA, 2-QQVGA)
OK	
>AT#CAMCOL=0*	(camera color: 0-color, 1-grayscale)
OK	
>AT#CAMZOOM=0	(camera zoom: 0-x1, 1-x2, 2-x4)
OK	
>AT#CAMTXT=0*	(camera timestamp: 0-no, 1-time only, 2-data only, 3-time&data)
OK	

Taking an reading a photo:

>AT#CAMEN=1	(camera ON)
OK	
>AT#TPHOTO	(take photo)
OK	
>AT+OBJL?	(see photo dimension)
#OBJL: Snapshot,38900	(where 38900 is the file dimension in bytes of the photo taken)
OK	
>AT#RPHOTO	(download the photo)
...data.....	(where ...data... Correspond to the photo data in binary)
OK	
>AT#TPHOTO	} Repeating photo capture and download n times
OK	
>AT#RPHOTO	
...data.....	
OK	
>AT#CAMEN=0	(camera OFF)

*only Transchip camera




13 Mounting the GE863-QUAD / PY on the Application Board

13.1 General


The [Telit GE863-QUAD / PY module](#) has been designed in order to be compliant with a standard lead-free SMT process

13.2 Module Finishing & Dimensions

 

**GE863-QUAD
GE863-PY**

1vv0300715 Rev. 1 - 19/09/06

 


Surface finishing Ni/Au for all test pads

Lead-free Alloy:
Surface finishing Sn/Ag/Cu for all solder pads




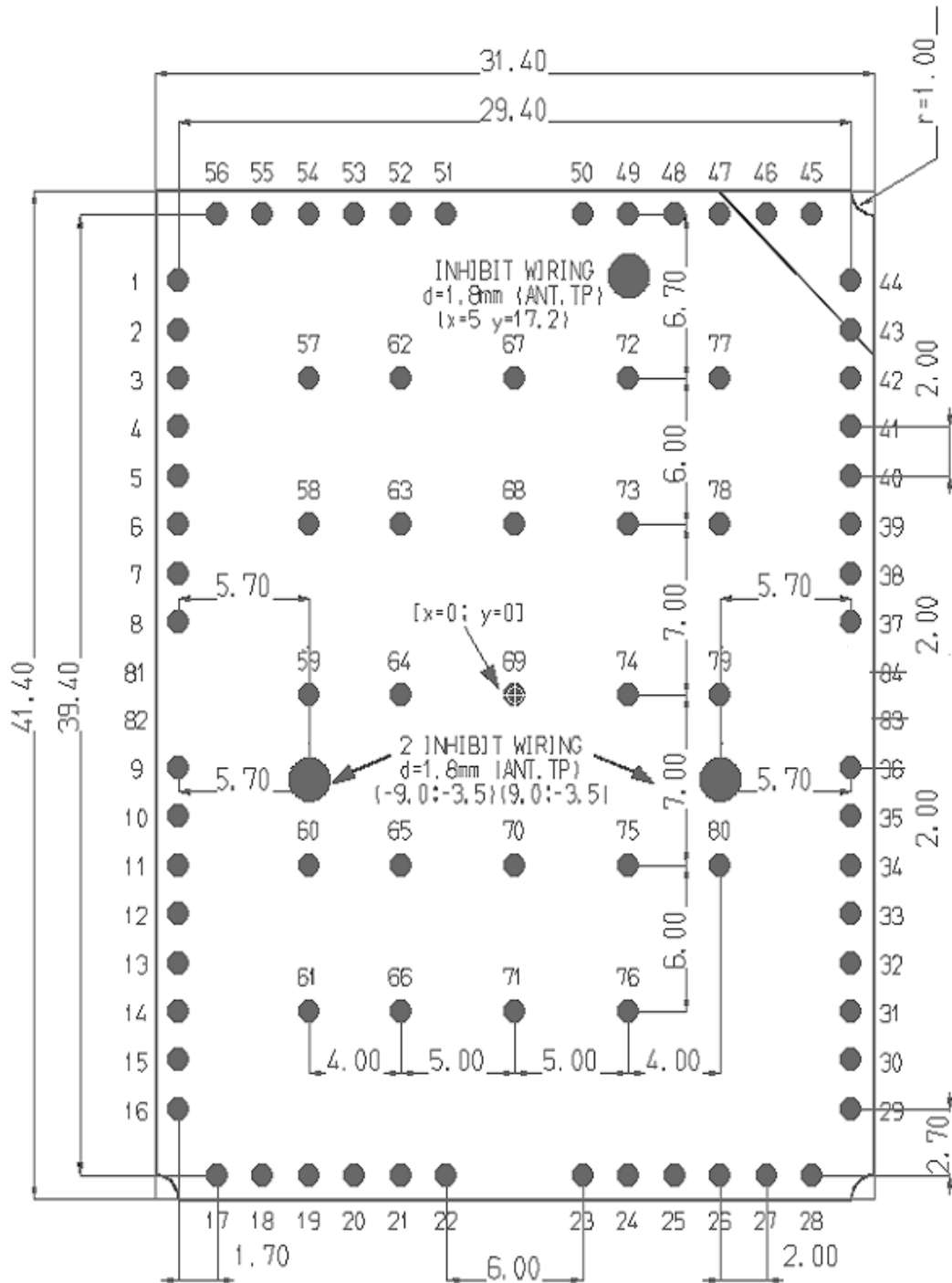13.2.1 Recommended foot print for the application




 13.2.7 Packing System

According to SMT processes for pick & place movement requirements, **Telit GE863-QUAD / PY modules** are packaged on trays, each tray contains 20 pieces. Tray dimensions are:




Note that trays can withstand a maximum temperature of 65° C.

 

**GE863-QUAD
GE863-PY**


1v0300715 Rev. 1 - 19/09/06

Modules orientation on tray:

 

Ref. Not rounded corner of module's printed board indicates pin 1 corner.

 The modules in the tray are oriented as shown in **A** and the tray is oriented toward left as shown in **B**.



15 SAFETY RECOMMENDATIONS

READ CAREFULLY

Be sure the use of this product is allowed in the country and in the environment required. The use of this product may be dangerous and has to be avoided in the following areas:

- Where it can interfere with other electronic devices in environments such as hospitals, airports, aircrafts, etc
- Where there is risk of explosion such as gasoline stations, oil refineries, etc

It is responsibility of the user to enforce the country regulation and the specific environment regulation.

Do not disassemble the product; any mark of tampering will compromise the warranty validity.

We recommend following the instructions of the hardware user guides for a correct wiring of the product. The product has to be supplied with a stabilized voltage source and the wiring has to be conforming to the security and fire prevention regulations.

The product has to be handled with care, avoiding any contact with the pins because electrostatic discharges may damage the product itself. Same cautions have to be taken for the SIM, checking carefully the instruction for its use. Do not insert or remove the SIM when the product is in power saving mode.

The system integrator is responsible of the functioning of the final product; therefore, care has to be taken to the external components of the module, as well as of any project or installation issue, because the risk of disturbing the GSM network or external devices or having impact on the security. Should there be any doubt, please refer to the technical documentation and the regulations in force.

Every module has to be equipped with a proper antenna with specific characteristics. The antenna has to be installed with care in order to avoid any interference with other electronic devices and has to guarantee a minimum distance from the body (20 cm). In case of this requirement cannot be satisfied, the system integrator has to assess the final product against the SAR regulation.

The European Community provides some Directives for the electronic equipments introduced on the market. All the relevant information's are available on the European Community website:

<http://europa.eu.int/comm/enterprise/rte/dir99-5.htm>

The text of the Directive 99/05 regarding telecommunication equipments is available, while the applicable Directives (Low Voltage and EMC) are available at:

http://europa.eu.int/comm/enterprise/electr_equipment/index_en.htm



